

(2)

If V is the potential difference across the resistor,
then, $V = IR$ ——— (2)

Now, work done to transfer charge (q) from A to B
is given as,

$$\text{work } (W) = qV \text{ ——— (3)}$$

From eqns. (1), (2) & (3), we get,

$$W = It \cdot IR$$

$$\therefore W = I^2 R t$$

since, electrical energy is converted into heat energy.

$$\therefore \boxed{\text{Heat developed } (H) = I^2 R t} \text{ ——— (4)}$$

Electrical power (P): \rightarrow Electrical power is defined as the
rate at which the work is done to maintain the steady
current in an electrical circuit.

$$\text{i.e. electrical power } (P) = \frac{W}{t}$$

$$= \frac{I^2 R t}{t}$$

$$\therefore \boxed{P = I^2 R} \text{ ——— (1)}$$

$$\boxed{P = \frac{V^2}{R}} \text{ ——— (2) } (\because I = \frac{V}{R})$$

$$\therefore \boxed{P = IV} \text{ ——— (3) } (\because V = IR)$$

Imp Electromotive force (Emf) \Rightarrow The emf of a cell is defined as the energy supplied by the source to the charge to move through an ~~air~~ electrical circuit.


The emf of a cell is the potential difference between two terminals of the cell in open circuit.

SI unit of E is volt (V).

Internal resistance (r) \Rightarrow The resistance offered by the source itself to the flow of current through it.

It is denoted by r .

In electrical circuit, the internal resistance is

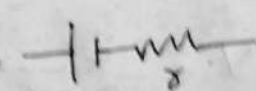written as,  .


Terminal potential difference (V) \Rightarrow The potential difference between two terminals of a cell in a closed circuit is called terminal potential difference.

The terminal potential difference is equal to the potential difference across external resistance in a circuit.

Its SI unit is volt (V)

Imp Relation between emf (E), terminal p.d. (V) and internal resistance (r) \Rightarrow

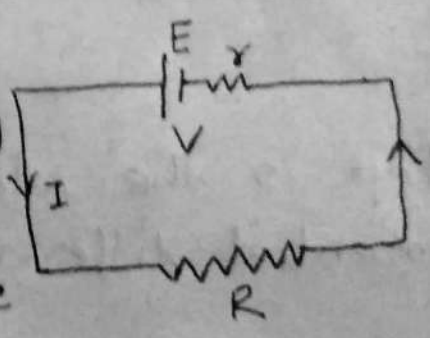Let, a cell of emf E and internal resistance r is connected in series with an external resistance R as shown in fig.



Let, I is the current flowing in the circuit.

Then, $E = IR + I\gamma$

$$E = I(R + \gamma)$$

$$\therefore I = \frac{E}{R + \gamma} \quad \text{————— ①}$$

Since, terminal potential difference is equal to the potential difference across external resistance.

Then, terminal p.d. (V) = IR

$$\therefore V = \frac{E}{R + \gamma} \times R$$

$$\therefore \frac{R + \gamma}{R} = \frac{E}{V}$$


$$\text{or, } 1 + \frac{\gamma}{R} = \frac{E}{V}$$

$$\text{or, } \frac{\gamma}{R} = \frac{E}{V} - 1$$

$$\text{or, } \frac{\gamma}{R} = \frac{E - V}{V}$$

$$\therefore \boxed{\gamma = \frac{(E - V)R}{V}} \quad \text{————— ②}$$

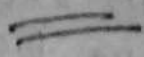This is the relation between emf (E), terminal potential difference (V) and internal resistance (γ).



①

Unit: 7.8: Resistance and heat,

Joule's law of heating :-

According to Joule, the heat developed in a conductor due to flow of current is,

i) directly proportional to the square of current

$$\text{i.e. } H \propto I^2 \quad \text{--- (1)}$$

ii) directly proportional to the resistance of conductor,

$$\text{i.e. } H \propto R \quad \text{--- (2)}$$

iii) directly proportional to the time for which current flows,

$$\text{i.e. } H \propto t \quad \text{--- (3)}$$

combining eqs (1), (2) & (3), we get,


$$H \propto I^2 R t$$

$$\therefore \boxed{H = \frac{I^2 R t}{J}} \quad \text{--- (4)}$$

where, J is constant known as Joule's mechanical equivalent of heat. J is conversion factor and its value is $4.18 \text{ Joule} \cdot \text{calorie}^{-1}$.

Ques Expression of heat developed in a wire :-

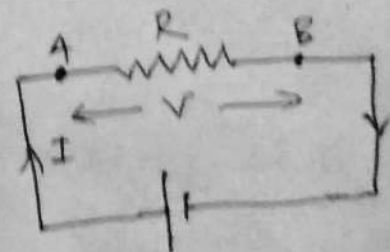Suppose, a resistance R between two points A and B as shown in fig. Let, I be the current flowing through it in a time t then,



$$I = \frac{q}{t} \quad ; \quad \text{where, } q = \text{charge}$$

$$\therefore q = It \quad \text{--- (1)}$$